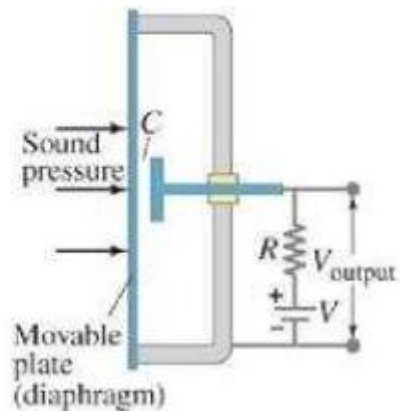


11. For what use are batteries connected in series? For what use are they connected in parallel? Does it matter if the batteries are nearly identical or not in either case?

14. In an  $RC$  circuit, current flows from the battery until the capacitor is completely charged. Is the total energy supplied by the battery equal to the total energy stored by the capacitor? If not, where does the extra energy go?

16. Figure 26–35 is a diagram of a capacitor (or condenser) **microphone**. The changing air pressure in a sound wave causes one plate of the capacitor  $C$  to move back and forth. Explain how a current of the same frequency as the sound wave is produced.



**FIGURE 26–35** Diagram of a capacitor microphone. Question 16.

11. When batteries are connected in series, their emfs add together, producing a larger potential. The batteries do not need to be identical in this case. When batteries are connected in parallel, the currents they can generate add together, producing a larger current over a longer time period. Batteries in this case need to be nearly identical, or the battery with the larger emf will end up charging the battery with the smaller emf.

14. No. As current passes through the resistor in the  $RC$  circuit, energy is dissipated in the resistor. Therefore, the total energy supplied by the battery during the charging is the combination of the energy dissipated in the resistor and the energy stored in the capacitor.

16. The capacitance of a parallel plate capacitor is inversely proportional to the distance between the plates:  $(C = \epsilon_0 A/d)$ . As the diaphragm moves in and out, the distance between the plates changes and therefore the capacitance changes with the same frequency. This changes the amount of charge that can be stored on the capacitor, creating a current as the capacitor charges or discharges. The current oscillates with the same frequency as the diaphragm, which is the same frequency as the incident sound wave, and produces an oscillating  $V_{\text{output}}$ .


4. (II) What is the internal resistance of a 12.0-V car battery whose terminal voltage drops to 8.4 V when the starter draws 95 A? What is the resistance of the starter?

4. See Figure 26-2 for a circuit diagram for this problem. Use Eq. 26-1.

$$V_{ab} = \mathcal{E} - Ir \rightarrow r = \frac{\mathcal{E} - V_{ab}}{I} = \frac{12.0 \text{ V} - 8.4 \text{ V}}{95 \text{ A}} = \boxed{0.038 \Omega}$$

$$V_{ab} = IR \rightarrow R = \frac{V_{ab}}{I} = \frac{8.4 \text{ V}}{95 \text{ A}} = \boxed{0.088 \Omega}$$

16. (II) Determine (a) the equivalent resistance of the circuit shown in Fig. 26-39, and (b) the voltage across each resistor.

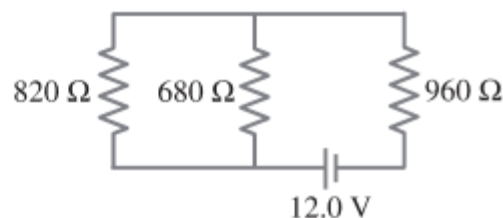

**FIGURE 26-39**  
Problem 16.

16. (a) The equivalent resistance is found by combining the 820 Ω and 680 Ω resistors in parallel, and then adding the 960 Ω resistor in series with that parallel combination.

$$R_{\text{eq}} = \left( \frac{1}{820 \Omega} + \frac{1}{680 \Omega} \right)^{-1} + 960 \Omega = 372 \Omega + 960 \Omega = 1332 \Omega \approx \boxed{1330 \Omega}$$

- (b) The current delivered by the battery is  $I = \frac{V}{R_{\text{eq}}} = \frac{12.0 \text{ V}}{1332 \Omega} = 9.009 \times 10^{-3} \text{ A}$ . This is the


current in the 960 Ω resistor. The voltage across that resistor can be found by Ohm's law.

$$V_{470} = IR = (9.009 \times 10^{-3} \text{ A})(960 \Omega) = 8.649 \text{ V} \approx \boxed{8.6 \text{ V}}$$

Thus the voltage across the parallel combination must be  $12.0 \text{ V} - 8.6 \text{ V} = \boxed{3.4 \text{ V}}$ . This is the voltage across both the 820 Ω and 680 Ω resistors, since parallel resistors have the same voltage across them. Note that this voltage value could also be found as follows.

$$V_{\text{parallel}} = IR_{\text{parallel}} = (9.009 \times 10^{-3} \text{ A})(372 \Omega) = 3.351 \text{ V} \approx 3.4 \text{ V}$$


19. (II) What is the net resistance of the circuit connected to the battery in Fig. 26-41?

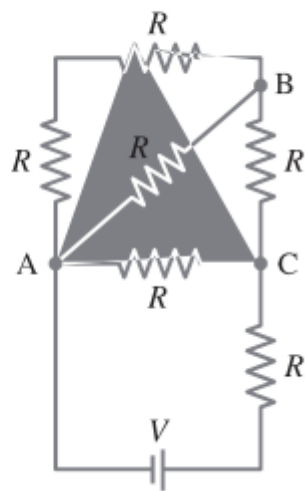


**FIGURE 26-41**  
Problems 19 and 20.

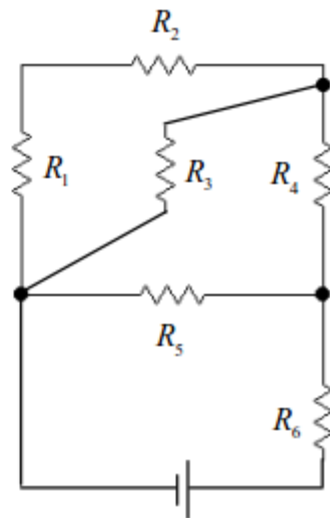19. The resistors have been numbered in the accompanying diagram to help in the analysis.  $R_1$  and  $R_2$  are in series with an equivalent resistance of  $R_{12} = R + R = 2R$ . This combination is in parallel with  $R_3$ , with an equivalent resistance of  $R_{123} = \left(\frac{1}{R} + \frac{1}{2R}\right)^{-1} = \frac{2}{3}R$ . This combination is in series with  $R_4$ , with an equivalent resistance of  $R_{1234} = \frac{2}{3}R + R = \frac{5}{3}R$ . This combination is in parallel with  $R_5$ , with an equivalent resistance of  $R_{12345} = \left(\frac{1}{R} + \frac{3}{5R}\right)^{-1} = \frac{5}{8}R$ . Finally, this combination is in series with  $R_6$ , and we calculate the final equivalent resistance.

$$R_{\text{eq}} = \frac{5}{8}R + R = \boxed{\frac{13}{8}R}$$



31. (II) (a) What is the potential difference between points a and d in Fig. 26-49 (similar to Fig. 26-13, Example 26-9), and (b) what is the terminal voltage of each battery?

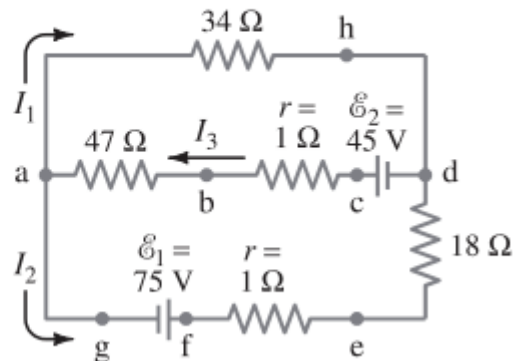

**FIGURE 26-49**  
Problem 31.

31. This circuit is identical to Example 26-9 and Figure 26-13 except for the numeric values. So we may copy the same equations as developed in that Example, but using the current values.

$$\text{Eq. (a): } I_3 = I_1 + I_2 \quad ; \quad \text{Eq. (b): } -34I_1 + 45 - 48I_3 = 0$$

$$\text{Eq. (c): } -34I_1 + 19I_2 - 75 = 0 \quad \text{Eq. (d): } I_2 = \frac{75 + 34I_1}{19} = 3.95 + 1.79I_1$$

$$\text{Eq. (e): } I_3 = \frac{45 - 34I_1}{48} = 0.938 - 0.708I_1$$

$$I_3 = I_1 + I_2 \rightarrow 0.938 - 0.708I_1 = I_1 + 3.95 + 1.79I_1 \rightarrow I_1 = -0.861 \text{ A}$$

$$I_2 = 3.95 + 1.79I_1 = 2.41 \text{ A} \quad ; \quad I_3 = 0.938 - 0.708I_1 = 1.55 \text{ A}$$

31. (II) (a) What is the potential difference between points a and d in Fig. 26-49 (similar to Fig. 26-13, Example 26-9), and (b) what is the terminal voltage of each battery?

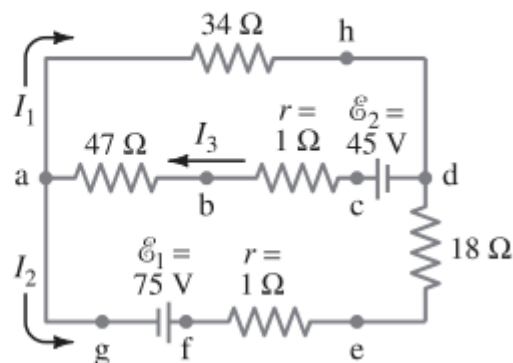


FIGURE 26-49  
Problem 31.

44. (II) In Fig. 26-58 (same as Fig. 26-17a), the total resistance is  $15.0 \text{ k}\Omega$ , and the battery's emf is  $24.0 \text{ V}$ . If the time constant is measured to be  $24.0 \mu\text{s}$ , calculate (a) the total capacitance of the circuit and (b) the time it takes for the voltage across the resistor to reach  $16.0 \text{ V}$  after the switch is closed.

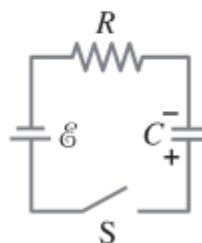


FIGURE 26-58  
Problems 44 and 46.

- (a) To find the potential difference between points a and d, start at point a and add each individual potential difference until reaching point d. The simplest way to do this is along the top branch.

$$V_{ad} = V_d - V_a = -I_1(34 \Omega) = -(-0.861 \text{ A})(34 \Omega) = 29.27 \text{ V} \approx \boxed{29 \text{ V}}$$

Slight differences will be obtained in the final answer depending on the branch used, due to rounding. For example, using the bottom branch, we get the following.

$$V_{ad} = V_d - V_a = \mathcal{E}_1 - I_2(19 \Omega) = 75 \text{ V} - (2.41 \text{ A})(19 \Omega) = 29.21 \text{ V} \approx 29 \text{ V}$$

- (b) For the  $75\text{-V}$  battery, the terminal voltage is the potential difference from point g to point e. For the  $45\text{-V}$  battery, the terminal voltage is the potential difference from point d to point b.

$$75 \text{ V battery: } V_{\text{terminal}} = \mathcal{E}_1 - I_2 r = 75 \text{ V} - (2.41 \text{ A})(1.0 \Omega) = \boxed{73 \text{ V}}$$

$$45 \text{ V battery: } V_{\text{terminal}} = \mathcal{E}_2 - I_3 r = 45 \text{ V} - (1.55 \text{ A})(1.0 \Omega) = \boxed{43 \text{ V}}$$

44. (a) From Eq. 26-7 the product  $RC$  is equal to the time constant.

$$\tau = RC \rightarrow C = \frac{\tau}{R} = \frac{24.0 \times 10^{-6} \text{ s}}{15.0 \times 10^3 \Omega} = \boxed{1.60 \times 10^{-9} \text{ F}}$$


- (b) Since the battery has an EMF of  $24.0 \text{ V}$ , if the voltage across the resistor is  $16.0 \text{ V}$ , the voltage across the capacitor will be  $8.0 \text{ V}$  as it charges. Use the expression for the voltage across a charging capacitor.

$$V_C = \mathcal{E}(1 - e^{-t/\tau}) \rightarrow e^{-t/\tau} = \left(1 - \frac{V_C}{\mathcal{E}}\right) \rightarrow -\frac{t}{\tau} = \ln\left(1 - \frac{V_C}{\mathcal{E}}\right) \rightarrow$$

$$t = -\tau \ln\left(1 - \frac{V_C}{\mathcal{E}}\right) = -(24.0 \times 10^{-6} \text{ s}) \ln\left(1 - \frac{8.0 \text{ V}}{24.0 \text{ V}}\right) = \boxed{9.73 \times 10^{-6} \text{ s}}$$



79. In the circuit shown in Fig. 26–68, the  $33\text{-}\Omega$  resistor dissipates  $0.80\text{ W}$ . What is the battery voltage?

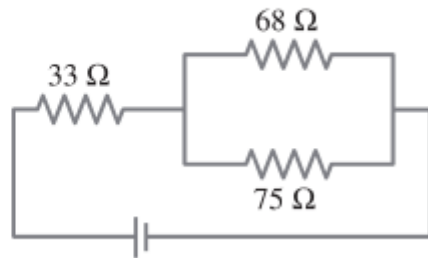


**FIGURE 26–68**  
Problem 79.

79. The current in the circuit can be found from the resistance and the power dissipated. Then the product of that current and the equivalent resistance is equal to the battery voltage.

$$P = I^2 R \rightarrow I = \sqrt{\frac{P_{33}}{R_{33}}} = \sqrt{\frac{0.80\text{ W}}{33\Omega}} = 0.1557\text{ A}$$

$$R_{\text{eq}} = 33\Omega + \left( \frac{1}{68\Omega} + \frac{1}{75\Omega} \right)^{-1} = 68.66\Omega \quad V = IR_{\text{eq}} = (0.1557\text{ A})(68.66\Omega) = 10.69\text{ V} \approx \boxed{11\text{ V}}$$

83. A flashlight bulb rated at  $2.0\text{ W}$  and  $3.0\text{ V}$  is operated by a  $9.0\text{-V}$  battery. To light the bulb at its rated voltage and power, a resistor  $R$  is connected in series as shown in Fig. 26–72. What value should the resistor have?

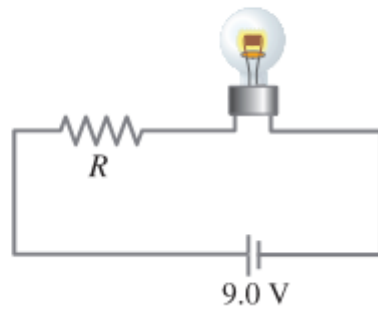

**FIGURE 26–72**  
Problem 83.

83. Write Kirchhoff's loop rule for the circuit, and substitute for the current and the bulb resistance based on the bulb ratings.

$$P_{\text{bulb}} = \frac{V_{\text{bulb}}^2}{R_{\text{bulb}}} \rightarrow R_{\text{bulb}} = \frac{V_{\text{bulb}}^2}{P_{\text{bulb}}} \quad P_{\text{bulb}} = I_{\text{bulb}} V_{\text{bulb}} \rightarrow I_{\text{bulb}} = \frac{P_{\text{bulb}}}{V_{\text{bulb}}}$$

$$\mathcal{E} - I_{\text{bulb}} R - I_{\text{bulb}} R_{\text{bulb}} = 0 \rightarrow$$

$$R = \frac{\mathcal{E}}{I_{\text{bulb}}} - R_{\text{bulb}} = \frac{\mathcal{E}}{P_{\text{bulb}}/V_{\text{bulb}}} - \frac{V_{\text{bulb}}^2}{P_{\text{bulb}}} = \frac{V_{\text{bulb}}}{P_{\text{bulb}}} (\mathcal{E} - V_{\text{bulb}}) = \frac{3.0\text{ V}}{2.0\text{ W}} (9.0\text{ V} - 3.0\text{ V}) = \boxed{9.0\Omega}$$

\*91. Measurements made on circuits that contain large resistances can be confusing. Consider a circuit powered by a battery  $\mathcal{E} = 15.000 \text{ V}$  with a  $10.00\text{-M}\Omega$  resistor in series with an unknown resistor  $R$ . As shown in Fig. 26–80, a particular voltmeter reads  $V_1 = 366 \text{ mV}$  when connected across the  $10.00\text{-M}\Omega$  resistor, and this meter reads  $V_2 = 7.317 \text{ V}$  when connected across  $R$ . Determine the value of  $R$ . [Hint: Define  $R_V$  as the voltmeter's internal resistance.]

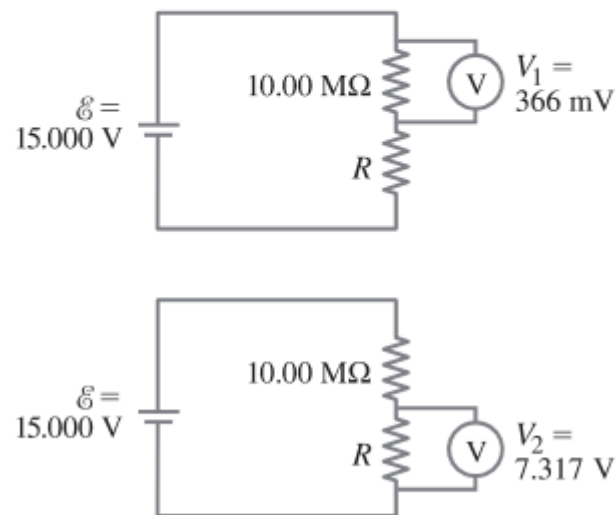


FIGURE 26–80 Problem 91.

91. We represent the  $10.00\text{-M}\Omega$  resistor by  $R_{10}$ , and the resistance of the voltmeter as  $R_V$ . In the first configuration, we find the equivalent resistance  $R_{\text{eqA}}$ , the current in the circuit  $I_A$ , and the voltage drop across  $R$ .

$$R_{\text{eqA}} = R + \frac{R_{10}R_V}{R_{10} + R_V} ; I_A = \frac{\mathcal{E}}{R_{\text{eqA}}} ; V_R = I_A R = \mathcal{E} - V_A \rightarrow \mathcal{E} \frac{R}{R_{\text{eqA}}} = \mathcal{E} - V_A$$

In the second configuration, we find the equivalent resistance  $R_{\text{eqB}}$ , the current in the circuit  $I_B$ , and the voltage drop across  $R_{10}$ .

$$R_{\text{eqB}} = R_{10} + \frac{RR_V}{R + R_V} ; I_B = \frac{\mathcal{E}}{R_{\text{eqB}}} ; V_{R_{10}} = I_B R_{10} = \mathcal{E} - V_B \rightarrow \mathcal{E} \frac{R_{10}}{R_{\text{eqB}}} = \mathcal{E} - V_B$$

We now have two equations in the two unknowns of  $R$  and  $R_V$ . We solve the second equation for  $R_V$  and substitute that into the first equation. We are leaving out much of the algebra in this solution.

$$\mathcal{E} \frac{R}{R_{\text{eqA}}} = \mathcal{E} \frac{R}{R + \frac{R_{10}R_V}{R_{10} + R_V}} = \mathcal{E} - V_A ;$$

$$\mathcal{E} \frac{R_{10}}{R_{\text{eqB}}} = \mathcal{E} \frac{R_{10}}{R_{10} + \frac{RR_V}{R + R_V}} = \mathcal{E} - V_B \rightarrow R_V = \frac{V_B R_{10} R}{(\mathcal{E} R - V_B R_{10} - V_B R)}$$

$$\mathcal{E} - V_A = \mathcal{E} \frac{R}{R + \frac{R_{10}R_V}{R_{10} + R_V}} = \mathcal{E} \frac{R}{R + \frac{R_{10} \left[ \frac{V_B R_{10} R}{(\mathcal{E} R - V_B R_{10} - V_B R)} \right]}{R_{10} + \left[ \frac{V_B R_{10} R}{(\mathcal{E} R - V_B R_{10} - V_B R)} \right]}} \rightarrow$$

$$R = \frac{V_B}{V_A} R_{10} = \frac{7.317 \text{ V}}{0.366 \text{ V}} (10.00 \text{ M}\Omega) = 199.92 \text{ M}\Omega \approx \boxed{200 \text{ M}\Omega} \quad (3 \text{ sig. fig.})$$